

Figure 2.1 Impedances in three-phase wye (a) and delta (b) circuits.

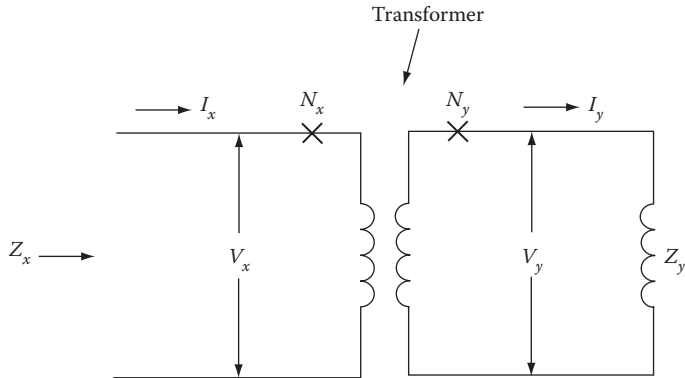


Figure 2.2 Impedances through one phase of a three-phase transformer.

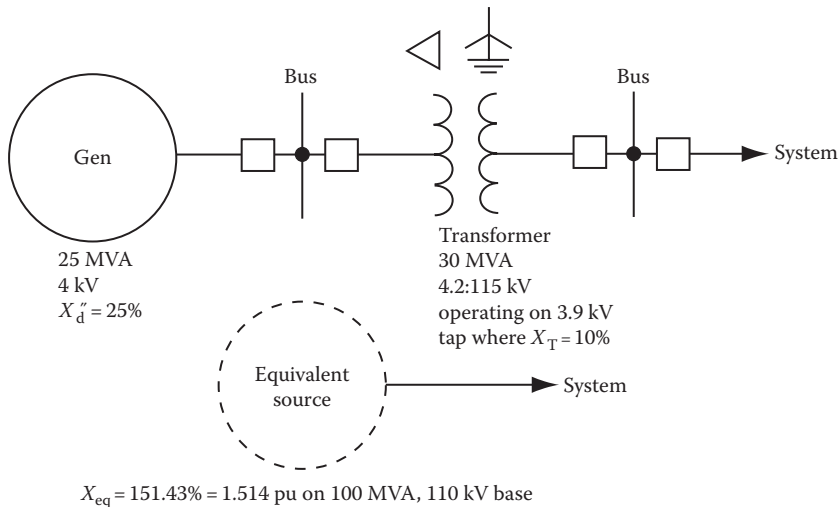


Figure 2.3 Typical example for combining a generator and a transformer into an equivalent source.